

Experiment 2 - Sequential Synthesis and FPGA Device Programming

Amirhossein Tayebi 810198430

Armin Eslami 810198349

Abstract— This document is about designing and implementing an interaction mechanism using the Cyclone II board

Keywords—state machine design

I. SERIAL TRANSMITTER

A. Onepulser

The Moore state machine design of the onepulser, the Verilog code and the testbench results are shown in fig. 1, fig. 2 and fig. 3.

OnePulser States:

 


Fig. 1: The moore state machine design of Onepulser

```
module OnePulser(input Clk,ClkPB,output reg ClkEn);
    reg [1:0] ps,ns;
    always@(ClkPB,ps)begin
        ClkEn=0;
        ns=0;
        case(ps)
            0:begin ns= ClkPB ? 1:0;ClkEn=0;end
            1:begin ns= 2; ClkEn=1; end
            2: ns=ClkPB? 2:0;
            default ns=0;
        endcase
    end
    always@(posedge Clk) ps<=ns;
endmodule
```

Fig. 2: The Verilog code of Onepulser

 


Fig. 3: Testbench waveform of Onepulser module

B. Orthogonal Finite State Machine

The moore state machine design of sequence detector and counter , the Verilog code and the testbench results are shown in fig. 4, fig. 5, fig. 6 and fig. 7.

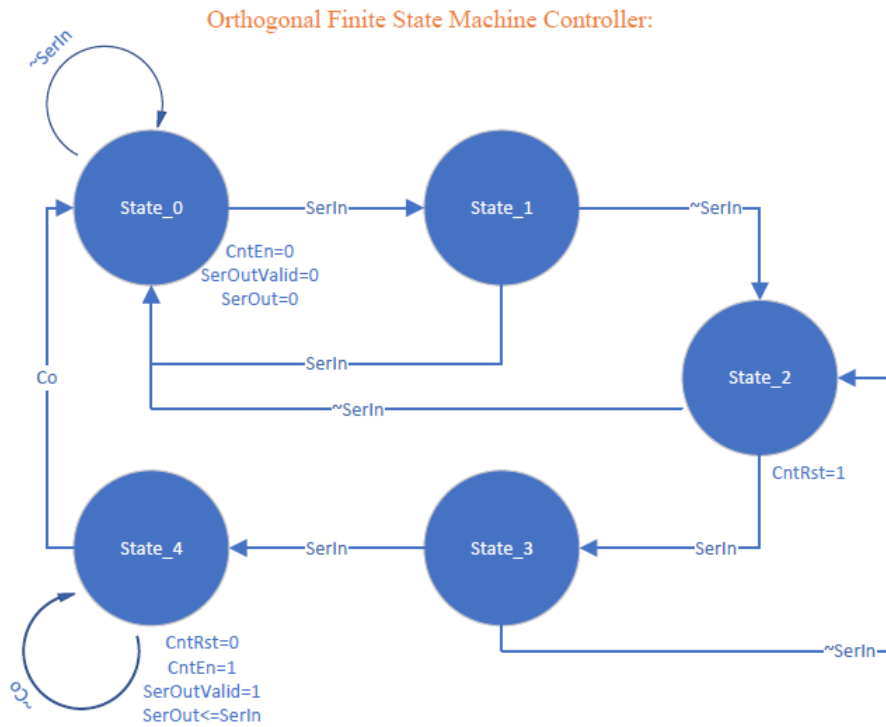


Fig. 4: The moore state machine design of OthFSM

```

module OthFSMCtrl(input Clk,Rst,input SerIn,ClkEn,Co,output reg SerOut,SerOutValid,CntEn,CntRst);
    reg [3:0] ps,ns;
    always@(ps,SerIn,Co)begin
        {SerOut,SerOutValid,CntEn,CntRst}=4'b0000;
        case(ps)
            1: begin ns= SerIn? 3:1;end
            3: begin ns= SerIn? 1:5; end
            5: begin ns=SerIn? 7:1;CntRst=1; end
            7: begin if(SerIn) begin
                    ns=8;CntRst=0;
                end
            end
            else ns=5;end
            8: begin ns=Co? 1:8; CntEn=1;SerOutValid=1;SerOut<=SerIn;end
            default: ns=1;
        endcase
    end
    always@(posedge Clk,posedge Rst)begin
        if(Rst) ps=1;
        else if (ClkEn) ps<=ns;
    end
endmodule

```

Fig. 5: The Verilog code of OthFSM controller

```

module Counter(input Clk,Rst,input ClkEn,CntEn,CntRst,output reg Co,output reg [3:0]CntOut);
    always@(posedge Clk)begin
        if(Rst) CntOut=0;
        else if (ClkEn)begin if (CntEn) CntOut<=CntOut+4'd1; end
    end
    assign Co=(CntOut[3])&(~CntOut[2])&(CntOut[1])&(~CntOut[0]);
endmodule

```

Fig. 6: The Verilog code of OthFSM counter

 


Fig. 7: The testbench waveform of OthFSM module

C. Seven Segment Display

The Verilog code of the seven segment display is shown in fig. 8.

```

module sev_segment(input clk, input [3:0]d , output reg [6:0] seg);
    always @(d,clk) begin
        case(d)
            4'd0: seg <= 7'b1000000;
            4'd1: seg <= 7'b1111001;
            4'd2: seg <= 7'b0100100;
            4'd3: seg <= 7'b0110000;
            4'd4: seg <= 7'b0011001;
            4'd5: seg <= 7'b0010010;
            4'd6: seg <= 7'b0000010;
            4'd7: seg <= 7'b1111000;
            4'd8: seg <= 7'b0000000;
            4'd9: seg <= 7'b0010000;
            default: seg <= 7'b1111111;
        endcase
    end
endmodule

```

Fig. 8: The Verilog code of OthFSM counter

And the top layer wiring is shown in fig. 9.

```

module OthFSM( input clk,rst,clkPB,SerIn,output reg SerOut, SerOutValid, output reg [6:0] reg10);

    wire clk_EN;
    wire[3:0] Count_out;
    OthFSMmini m1(clk,rst,SerIn,clk_EN,SerOut,SerOutValid,Count_out);
    OnePulser m2(clk,clkPB,clk_EN);
    sev_segment m3(clk,Count_out,reg10);
endmodule

```

Fig. 9: The Verilog code of OthFSM module

II. SERIAL TRANSMITTER IMPLEMENTATION

We are using DE1 development board for our design implementation. The RTL design, Board

image and wiring setup are shown in fig. 10, fig. 11, fig. 12.

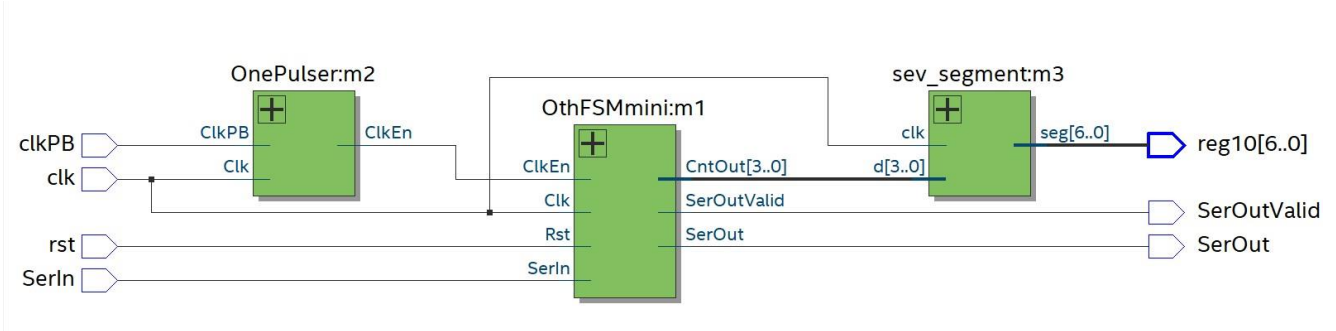


Fig. 10: The RTL design of OthFSM module

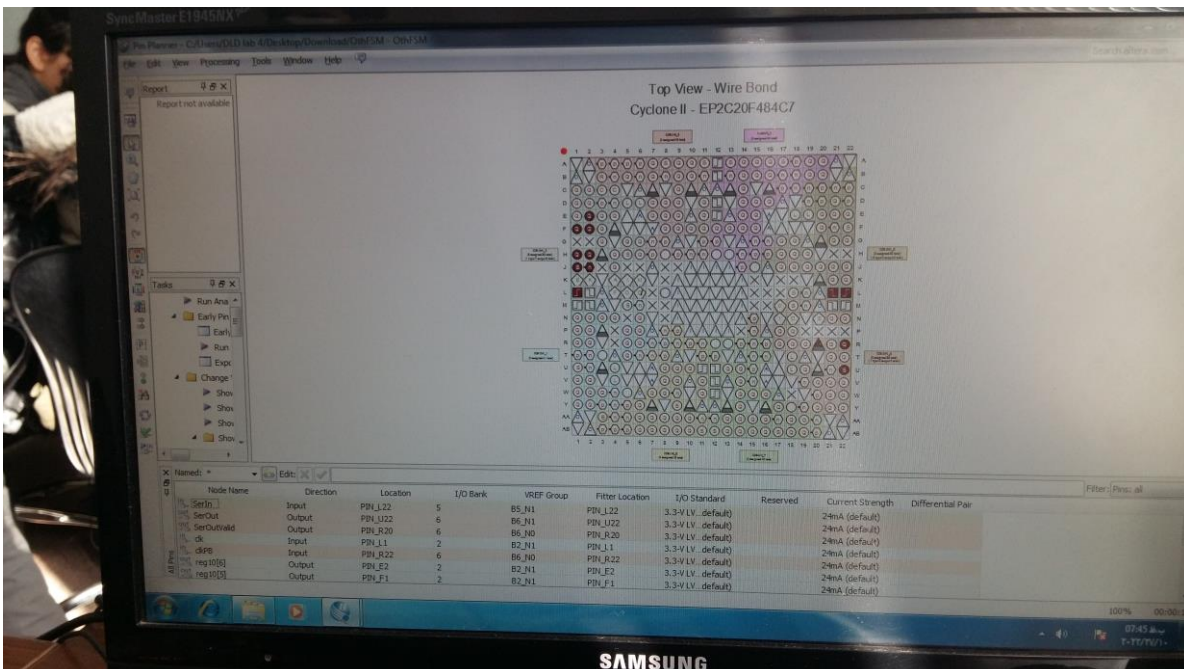


Fig. 11: The wiring view of DE1 board

 


Fig. 12: A glance of DE1 board while executing the program